

CS:Technical::Electrical

Unit prefixes

Unit prefixes

symbol	name	factor
<i>T</i>	tera	$\cdot 10^{12}$
<i>G</i>	giga	$\cdot 10^9$
<i>M</i>	mega	$\cdot 10^6$
<i>k</i>	kilo	$\cdot 10^3$
	1	$\cdot 10^0$
<i>m</i>	milli	$\cdot 10^{-3}$
μ	mikro	$\cdot 10^{-6}$
<i>n</i>	nano	$\cdot 10^{-9}$
<i>p</i>	piko	$\cdot 10^{-12}$
<i>f</i>	femto	$\cdot 10^{-15}$
<i>a</i>	atto	$\cdot 10^{-18}$

Charge

test

Charge is a property of elementary particles

- ↳ electrons, protons, pions, muons,
- ↳ there is positive and negative charge
- ↳ charge occurs only in discrete units
- ↳ some particles don't have charge (neutrons, photons,...)

The unit for charge is the coulomb C

The unit load is $e = 1.602176634 \cdot 10^{-19} C$

One coulomb requires about $6.25 \cdot 10^{18}$ electrons

Analogy for charge is amount of water (litres, kg)

0.1 Current

Current (symbol usually I) is the flow of charge Q , i.e. charge per time: $I = Q/T$ or, more precisely, $I = dQ/dt$

The unit for current is ampere A

At $1A$, 1 coulomb flows through a wire per second

1nA

1μA

0.2 Voltage

Voltage is the difference in electrical potentials

Strom in einem
'kleinen' Transistor
auf einem Chip
↳ i.e. the energy required to move a unit charge in an electric field

Leckstrom
in einem
Photosensor

Versorgung
(langsam
einfach
the unit for voltage is volt V
Analogy for voltage is water level / pressure (Pa)

1 μ V

1mV

0.3 Ground

Ground is a reference potential to which we relate all voltages
A synonym for ground is mass

$$\sum_{k=1}^n U_k = 0$$

Follows from conservation of energy

switch symbols are:

0.4 Kirchhoff's laws

node rule: The sum of all currents in a node is zero

$$\sum_{k=1}^n I_k = 0$$

0.5 Power

In order to maintain a current flow, energy must be constantly expended.

The required power is $P = U \cdot I$

The unit for power is W watt

0.6 Energy

The (electric) energy is $E = P \cdot t$ (power over time)

The unit for energy is J joule

A full car 'battery' (accumulator) contains e.g. an energy of $50kWh = 50kW \cdot 1h = 50,000W \cdot 3,600s = 180MJ$

0.7 Resistors

A resistor is a component with 2 terminals that a current can flow through if a voltage is applied



The unit for resistance is Ω omega

If the current is proportional to the voltage, we call it ohmic resistor that holds:


Kleinsten Schritt
in einem 16 Bit
DAC (CD)

Follows from conservation of charge (charge cannot vanish).

(0.8-3.3V)

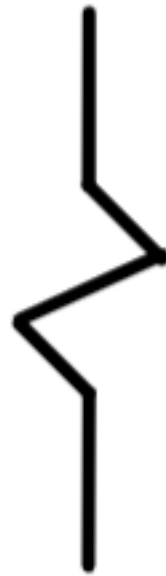
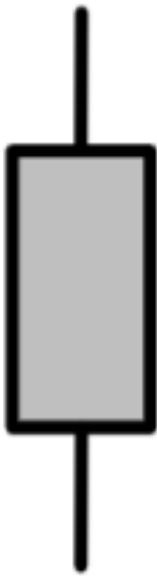


Switch symbols are:

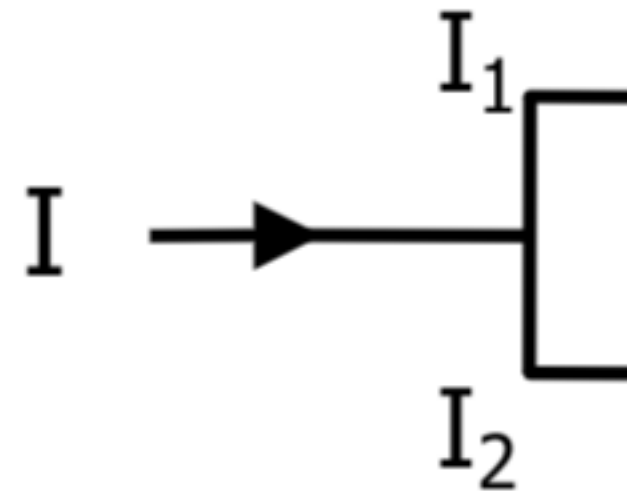

$$I = I_1 + I_2 = G_1 \times U$$

0.8 Voltage Divider

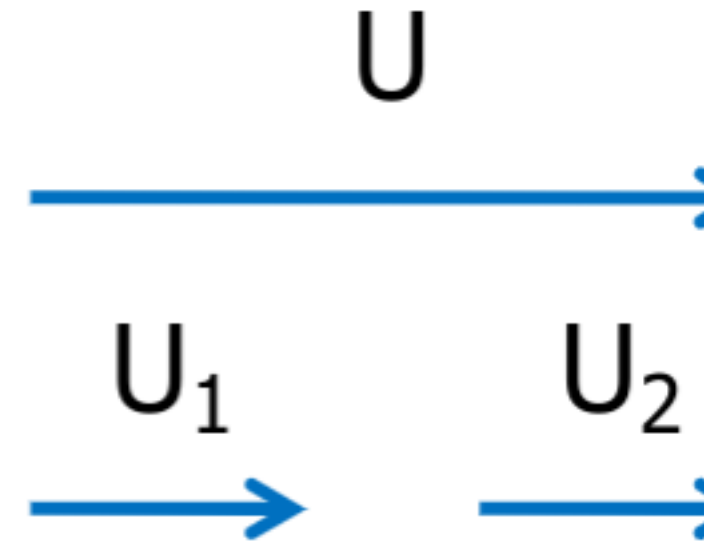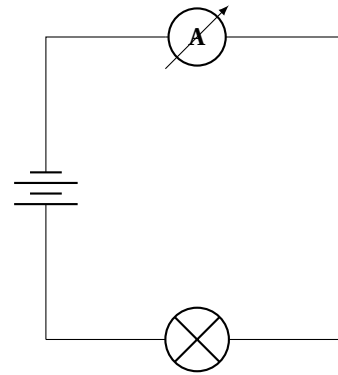

0.9 Capacitors / Capacitance

A capacitor can store charge (Q).

The unit for capacity is C farad

The capacity is $C = Q/U$

Analogy for capacitor is bathtub holding water level

Charge capacitor

↳ without resistor: $U(t) = \frac{I_0}{C} \cdot t$

↳ with resistor $U(t) = U_0 - U_0 e^{-\frac{t}{RC}}$



$$U = U_1 + U_2 = I \times R_1 + I \times R_2 =$$